

This product, formerly sold by ams AG, and before that optionally by either Applied Sensors GmbH, acam-messelectronic GmbH or Cambridge CMOS Sensors, is now owned and sold by

## ScioSense

The technical content of this document under ams / Applied Sensors / acammesselectronic / Cambridge CMOS Sensors is still valid.

Contact information Headquarters: Sciosense B.V. High Tech Campus 10 5656 AE Eindhoven The Netherlands info@sciosense.com www.sciosense.com





## acam-messelectronic gmbH

is now

## Member of the ams Group

The technical content of this acam-messelectronic document is still valid.

**Contact information:** 

Headquarters:

ams AG Tobelbader Strasse 30 8141 Premstaetten, Austria Tel: +43 (0) 3136 500 0 e-Mail: ams\_sales@ams.com

Please visit our website at www.ams.com



## TDC-GPX - Reduced Decoupling

This note is a supplement to application note no. 13, "TDC-GPX - PLL Regulation Circuit"

The intention is to show possibilities to reduce the number and size of the decoupling capacitors in the TDC-GPX supply circuit. We propose the following capacitors for the different power supply blocks:

1.	Vddo	Data bus I/O supply	TQFP pins 17, 40, 54 FBGA pins G3, L6, L12	100 nF per pin
2.	Vddo	I/O supply	TQFP pins 2,98,94,91,86,82,81,77 FBGA pins B1,A3,C4,C5,B7,A9,B9,A11	Connect all pins to a common copper plane and place two 100nF capacitors close to pins 77/A11 and 98/A3
3.	Vddc	Core supply	TQFP pins 1, 10, 39, 69, 79 FBGA pins A1, F1, M7, E12, B10	Connect a capacitor to each side of the chip TQFP pins 10, 39, 69, 79 FBGA pins F1, M7, E12, B10
			Standard: 4 x 47 $\mu$ F Derating (increase of standard deviation 4 x 10 $\mu$ F up to 200ns: no effect up to 500ns: about 4ps up to 1000ns: about 15ps	a) with smaller capacities: 4 x 22 μF up to 200ns: no effect up to 500ns: about 2 ps up to 1000ns: about 7 ps
4.	Vddc-o Vddc-h	Hardmacro supply	TQFP pins 87, 88 FBGA pins C6, A7	One capacitor to each pin and the voltage regulator output
			Standard: 1 x 100 $\mu$ F at regulator out and 2 x 47 $\mu$ F at the pinsThe regulator decoupling can be reduced to 10 $\mu$ F without a negative effectDerating (increase of standard deviation) with smaller capacities at the pins:2 x 10 $\mu$ F2 x 22 $\mu$ Fup to 200ns: no effectup to 200ns: no effectup to 500ns: about 4 psup to 500ns: about 2 psup to 1000ns: about 10 psup to 1000ns: about 5 ps	

